

A voltage-controlled oscillator based around the CEM3340 with an LFO switch.

Based on these designs:  
 - <https://www.lookmumnocomputer.com/projects#/cem-3340-diy-simple>  
 - <https://youtu.be/GsTG2V7tcU>

