

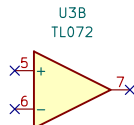
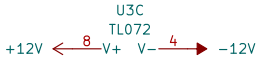
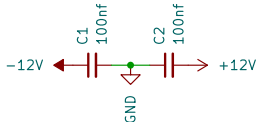


Voltage controlled filter with resonance dial and a high-pass/low-pass selector switch.

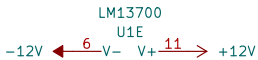Based off the design here:
<https://www.lookmumnocomputer.com/projects#/simple-filter>



Unused half of TL072

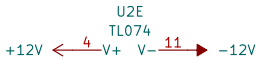