

A subset of the oscillator circuit with just enough to get the 3340 to do _anything_. Build this first before extending it into the full circuit so the circuit can be progressively built up and tested throughout the build. The triangle wave output should oscillate with noise.

